

You must show **all** your work! Answers without supporting work will not be given credit. Write answers in spaces provided. Illegible work falls under the *Intended Purpose* policy.

You must upload your submission as a SINGLE PDF DOCUMENT. Multiple file submissions or files of any other type will not be accepted.

This assignment is worth 10.0/60.0 ($\approx 17\%$) of Problem Assignment points

Name: _____

1. Show the truth table for a two-bit binary adder—that is a circuit with

- Four inputs, a_1, a_0, b_1, b_0 .
 - a_1a_0 and b_1b_0 represent two 2-bit unsigned binary integers
- Three outputs, c_{out}, s_1 and s_0 .
 - c_{out} represents a carry signal from the sum of the two 2-bit integers and
 - s_1s_0 represents the 2-bit unsigned binary sum of the two 2-bit integers.
- For credit, ensure you order your input $a_1a_0b_1b_0$ and
- Your output $c_{out}s_1s_0$.
- Notice there is no c_{in} . You're welcome! Why is this a *very good* thing from your point of view?

(1.0 Points)

2. For each of the following two expressions, select all of the following definitions [i, ii, iii, iv] which apply. **(1.0 points)**

- i. Product term iii. Sum term
ii. SoP expression iv. PoS expression

(a) $ab'cd'$

Answer:_____

(b) $a' + b + c' + d$

Answer:_____

3. Using properties 1 to 10, reduce the following expressions to a minimum SOP form. Show each step; the numbers of terms and literals in minimum form are shown in parentheses. **(1.0 points)**

(a) $x'y'z + x'yz + xy'z' + xyz'$ (2 terms, 4 literals)


(b) $w'x'y'z + wx'y'z + wx'yz + wxyz$ (2 terms, 6 literals)

(c) $w'x'y'z' + w'x'yz' + w'x'yz + wxy'z' + wxyz' + wxyz$ (4 terms, 12 literals)

4. Show a block diagram of a system using AND, OR, and NOT gates to implement the following functions. Your AND and OR gates have a fan-in of two (2). Assume that variables are available only uncomplemented (this means NOT gates are required when variables are complemented). **Do not manipulate the equation. (1.0 points)**

$$wxy'z' + vy(w+x)' + w'y$$

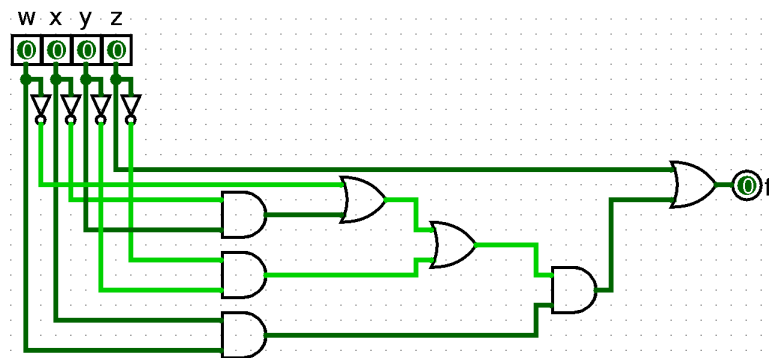5. Translate the following circuit into an algebraic expression, then put it in sum of product form. Write your final answer as $f(w, x, y, z) = \dots$ (1.0 points)



Answer: _____

Answer: _____

Cont.

6. Given the following function h , find the complement, h' . Only single variables may be complemented in the answer. **(1.0 points)**

$$h = ab'c + a'bc' + d(c' + a')(b' + a')$$

7. For each of the following functions:

$$f(a, b, c, d) = \Sigma m(1, 6, 9, 11, 15)$$

$$g(a, b, c, d) = \Sigma m(0, 6, 7, 8, 14)$$

- (a) Provide truth table for both f and g behavior.
- (b) Convert to an algebraic expression in sum of **minterms** form.

(1.0 Points)

8. Perform each of the following using only P8a, P8b, and P14.

(a) Convert the following PoS algebraic expression into SoP form. **(1.0 points)**

$$(b' + d')(a' + b + c)(b + c' + d)$$

- (b) Convert the following SoP algebraic expression into PoS form. **(1.0 points)**

$$w'xy' + w'x'y + wx'z$$

9. Draw, label, and fill in a Karnaugh Map for the following functions.

(a) Use the horizontal form of the 8-cell map we discussed in class:

$$f(x, y, z) = x'y + xz + yz.$$

You must circle and label the implicant(s) which correspond to each product term. **(0.5 points)**

(b) For the sum of Minterms, $f(a, b, c, d) = \Sigma m(1, 4, 9, 13)$. You need not circle the Minterms on your map. **(0.5 points)**